



# Sistem Telekomunikasi

---

Minggu ke-02




# Attenuator

---

- An attenuator is an electronic device that reduces the amplitude or power of a signal without appreciably distorting its waveform.
- An attenuator is effectively the opposite of an amplifier, though the two work by different methods. While an amplifier provides gain, an attenuator provides loss, or gain less than 1.
- Attenuators are usually passive devices made from simple voltage divider networks

# Pi-Attenuator

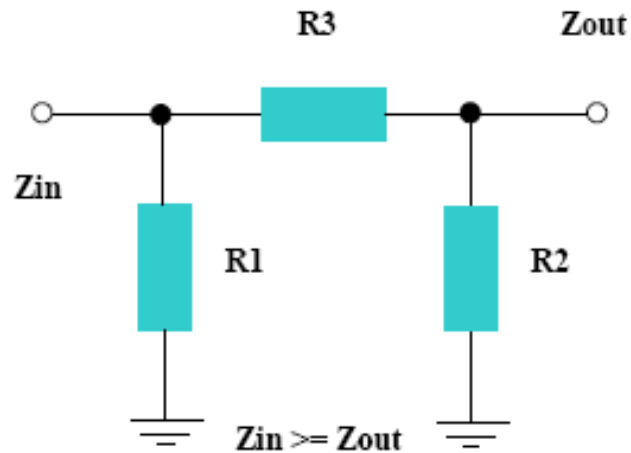

$$R3 = \frac{1}{2} \left( 10^{\frac{L}{10}} - 1 \right) \sqrt{\frac{Z_{in} * Z_{out}}{10^{\frac{L}{10}}}}$$

$$R2 = \frac{1}{\frac{10^{\frac{L}{10}} + 1}{Z_{out} \left( 10^{\frac{L}{10}} - 1 \right)} - \frac{1}{R3}}$$


$$R1 = \frac{1}{\frac{10^{\frac{L}{10}} + 1}{Z_{in} \left( 10^{\frac{L}{10}} - 1 \right)} - \frac{1}{R3}}$$

Where L = desired loss in dB

Zin = desired input impedance (ohms)

Zout = desired output impedance (ohms)

# T-Attenuator

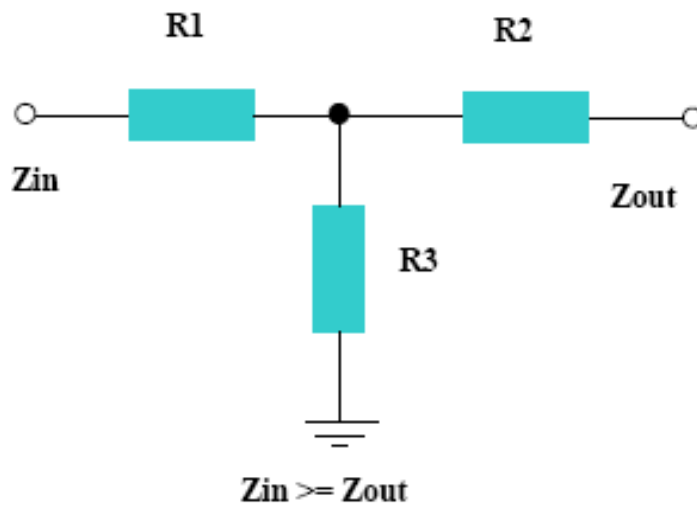

$$R3 = \frac{2\sqrt{Z_{in} * Z_{out} * 10^{\frac{L}{10}}}}{10^{\frac{L}{10}} - 1}$$

$$R2 = \frac{10^{\frac{L}{10}} + 1}{10^{\frac{L}{10}} - 1} Z_{out} - R3$$


$$R2 = \frac{10^{\frac{L}{10}} + 1}{10^{\frac{L}{10}} - 1} Z_{in} - R3$$

Where L = desired loss in dB

Zin = desired input impedance (ohms)

Zout = desired output impedance (ohms)

# Bridge T-Attenuator

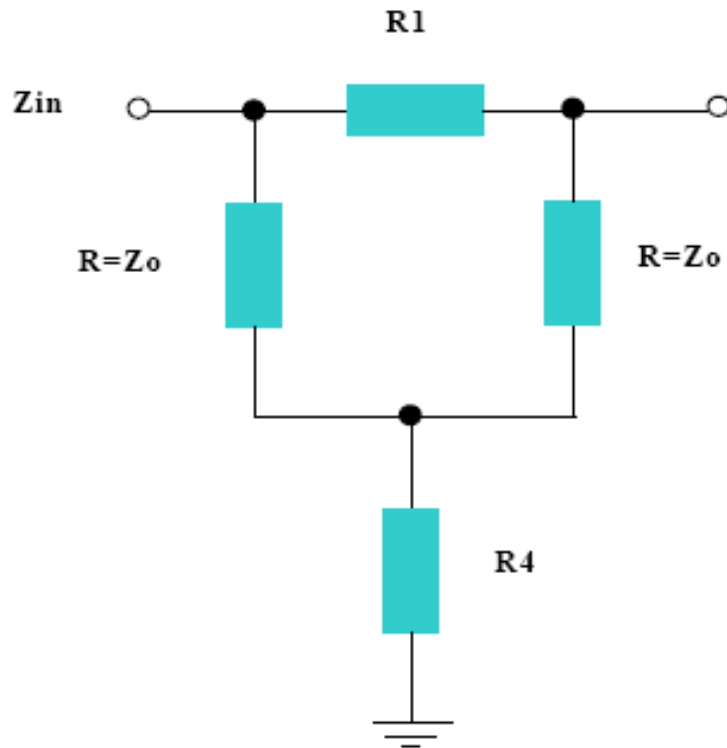

$$R1 = Z_o \left( 10^{\frac{L}{20}} - 1 \right)$$

$$R4 = \frac{Z_o}{10^{\frac{L}{20}} - 1}$$


Where  $L$  = desired loss in dB

$Z_{in}$  = desired input impedance (ohms)

$Z_{out}$  = desired output impedance (ohms)

$Z_o$  = Circuit characteristic impedance (ohms)

# Narrow Band Active Attenuator

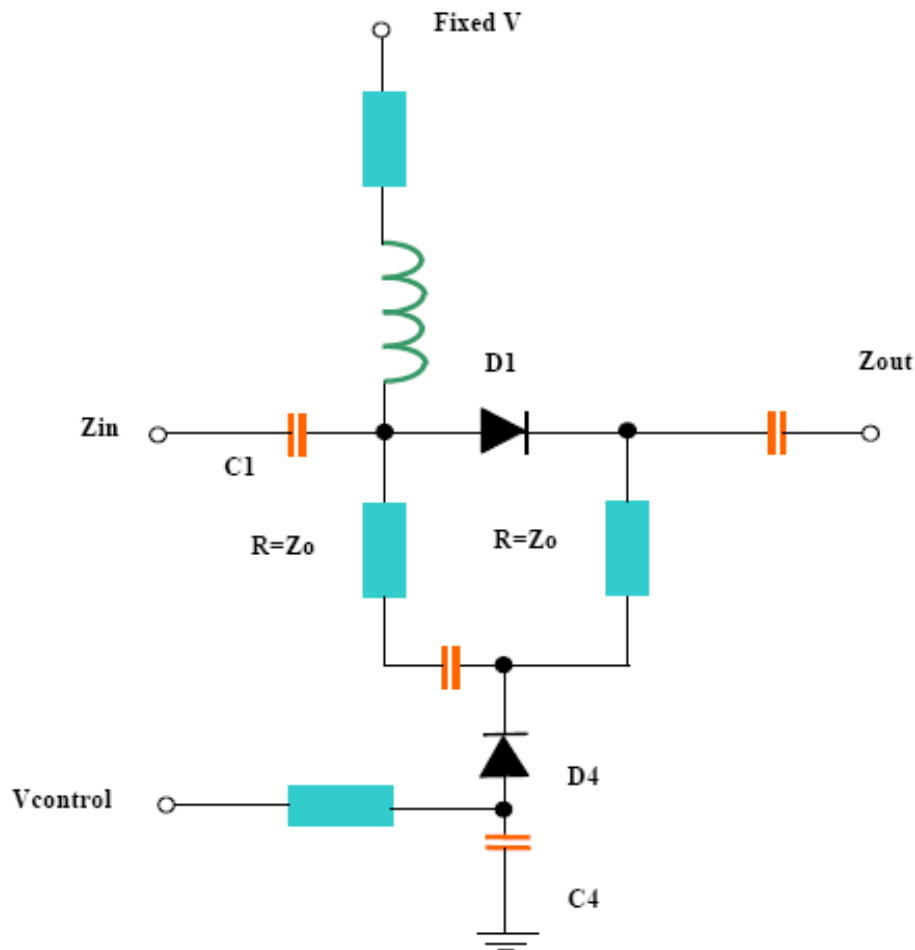

Minimumattenuation

$$L = 20\log\left(\frac{R1}{50} + 1\right) = 20\log\left(\frac{10}{50} + 1\right) = 1.58\text{dB approx}$$

Where L = desired loss in dB

Maximumattenuation

$$L = 20\log\left(\frac{R1}{50} + 1\right) = 20\log\left(\frac{1500}{50} + 1\right) = 29\text{dB approx}$$